

DESIGN &amp; TECHNOLOGY · Y3-Y6

# Electrical Systems

Knowledge Organiser — KS2 D&amp;T

## Key vocabulary

1

**Circuit**

A complete loop that lets electricity flow from a power source and back again.

2

**Component**

Each part in a circuit — battery, wire, bulb, switch, motor, buzzer.

3

**Battery**

The power source. Stores chemical energy and releases it as electrical energy.

4

**Wire**

The metal pathway electricity travels along.

5

**Switch**

Something you can press to OPEN (off) or CLOSE (on) a circuit.

6

**Bulb**

Lights up when electricity flows through it.

7

**Buzzer**

Makes a sound when electricity flows through it.

8

**Motor**

Spins when electricity flows — turns electrical energy into movement.



9

**Series circuit**

Components in one loop. If one fails, all stop working.

10

**Parallel circuit**

Two or more loops. If one fails, the others keep working.

## a circuit works

Electricity needs a complete

- Electricity flows from BATTERY → WIRE → COMPONENT → WIRE → BATTERY.
- If the loop is BROKEN at any point, nothing works.
- A switch creates a deliberate break that you can control.
- Wires must connect to BOTH ends of the battery (positive + and negative -).
- Most components have a positive and negative end — connect them the right way round.
- If your circuit doesn't work, check: is the loop complete? Is the switch on? Is the battery in correctly?

## non components

What each one does

- BATTERY (cell) — provides the power.
- WIRES — carry the electricity.
- BULB — lights up.
- BUZZER — makes a sound.
- MOTOR — spins something (a propeller, a wheel).
- LED — small light, only works one way round.
- SWITCH — turns the circuit on and off.
- RESISTOR — slows down the electricity, stops bulbs from burning out.



## Series vs Parallel

Two ways to wire components

- SERIES: all components in ONE loop. If one bulb breaks, ALL go out.
- Christmas lights used to be in series — one bulb out = whole string out.
- PARALLEL: each component on its OWN loop, sharing the battery. If one bulb breaks, the others stay on.
- Houses use parallel circuits — that's why turning off one light doesn't switch everything off.
- Parallel circuits use MORE BATTERY POWER but are more reliable.
- Series circuits make components DIMMER as you add more (the power is shared).

## Designing a product with a switch

What to think about

- PURPOSE: what should it do? (Light up at night? Buzz when opened?)
- USER: who is it for? Should it be easy to switch on?
- SWITCH TYPE: push button, slide, lever, magnetic?
- SAFETY: tape over wire ends, no exposed metal where fingers go.
- POWER: battery size — too small = won't light, too big = too heavy.
- TEST often. Most circuits don't work first time.
- Always disconnect the battery when not testing — saves the battery and prevents short circuits.

